

Computer Architecture 2024 fall Lab 1

1. Problem Description

In this homework, we are going to implement a simple RISC-V CPU with Verilog. The CPU in this homework is single-cycle, all operations are assumed to be completed equally in one cycle.

This CPU has 32 registers, and 1KB instruction memory. It should take 32-bit binary codes as input, and should do the corresponding RISC-V instructions, saving the result of arithmetic operations into the corresponding registers. Only arithmetic operations are covered in this homework, there will be no load/store instructions in this homework. We will examine the correctness of your implementation by dumping the value of each registers after each cycle.

1.1. Data path

Figure 1 describes the data path you should follow in this homework. The registers, PC, and instruction memory are provided by TAs, so you do not have to (and are also not allowed) modify them. The modules you have to implement is introduced in detail in section 1.6. And after you finish these modules, you have to connect these modules in your CPU.v.

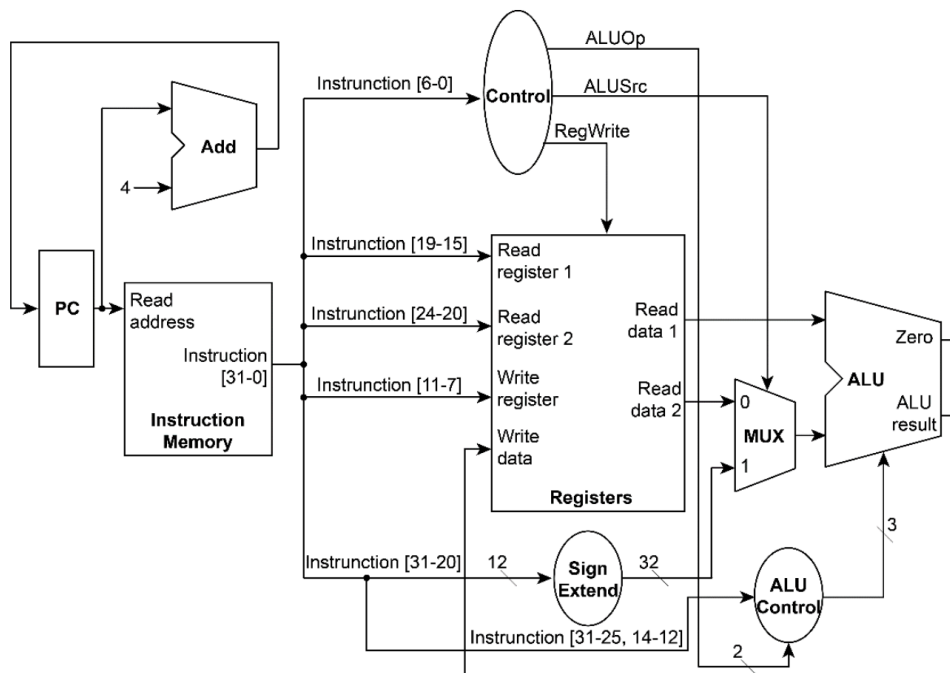


Figure 1 Data path of the CPU in this homework

1.2. Instructions

Your CPU should be able to support following instructions:

- `and rd, rs1, rs2` (bitwise and)
- `xor rd, rs1, rs2` (bitwise exclusive or)
- `sll rd, rs1, rs2` (shift left logically, `rs2` will always be positive in this lab)
- `add rd, rs1, rs2` (addition)
- `sub rd, rs1, rs2` (subtraction)

- `mul rd, rs1, rs2` (multiplication)
- `addi rd, rs1, imm` (addition)
- `srai rd, rs1, imm` (shift right arithmetically)

That is, to get full credits, your CPU have to function correctly upon encountering these instructions in any order. Instructions other than specified above will not be involved at evaluation.

1.3. Instruction Format

Instructions involved in this homework are 32-bit following RISC-V standard. Table below lists the specification of instructions your CPU should support in this homework.

funct7	rs2	rs1	funct3	rd	opcode	function
0000000	rs2	rs1	111	rd	0110011	and
0000000	rs2	rs1	100	rd	0110011	xor
0000000	rs2	rs1	001	rd	0110011	sll
0000000	rs2	rs1	000	rd	0110011	add
0100000	rs2	rs1	000	rd	0110011	sub
0000001	rs2	rs1	000	rd	0110011	mul
imm[11:0]		rs1	000	rd	0010011	addi
0100000	imm[4:0]	rs1	101	rd	0010011	srai

1.4. Input / Output Format

Besides the modules listed above, you are also provided “testbench.v” and “instruction.txt”. After you finish your modules and CPU, you should compile all of them including “testbench.v”. A recommended compilation command would be

```
$ iverilog -o CPU.out *.v
```

Then by default, your CPU loads “instruction.txt”, which should be placed at the same directory as CPU.out, into the instruction memory. This part is written in “testbench.v”. You don’t have to change it. “instruction.txt” is a plain text file which consists of 32 bits (ASCII 0 or 1) per line, representing one instruction per line. For example, the first 3 lines in “instruction.txt” are

```
0000000_00000_00000_000_01000_0110011 //add $t0,$0,$0
000000001010_00000_000_01001_0010011 //addi $t1,$0,10
000000001101_00000_000_01010_0010011 //addi $t2,$0,13
```

Note that underlines and texts after “//” (i.e. comments) are neglected. They are inserted simply for human readability. Therefore, the CPU should take “00000000000000000000000010000110011” and execute it in the first cycle, then “000000001010000000000010010010011” in the second cycle, and “000000001101000000000010100010011” in the third, and so on.

Also, if you include unchanged “testbench.v” into compilation, the program will generate a plain text file named “output.txt”, which dumps value of all registers at each cycle after execution. The file is self-explainable.

1.5. Machine code

Both R-type and I-type instructions are included in this homework. As we all know that they have different formats in RISC-V.

Name (Field size)	Field						Comments
	7 bits	5 bits	5 bits	3 bits	5 bits	7 bits	
R-type	funct7	rs2	rs1	funct3	rd	opcode	Arithmetic instruction format
I-type	immediate[11:0]		rs1	funct3	rd	opcode	Loads & immediate arithmetic

1.6. Modules

Following are modules you are required to implement and their function.

1.6.1. Control

Reads opcodes in the instruction and output control signals to control the behavior of ALU and registers.

1.6.2. ALU control

Reads funct7 and funct3 in the instruction and tell ALU what kind of operation it should do.

1.6.3. Sign extend

Signed extends the immediate value into 32-bit number. You have to make sure both positive and negative immediate values can work correctly.

1.6.4. ALU

According to the control signal, do the corresponding arithmetic operation on two input fields.

1.6.5. PC, Instruction memory, Registers, testbench

These modules are provided by TA. You are not allowed to modify them. (Except for adding debug information in testbench)

1.6.6. Others

You can add more modules than listed above if you want.

1.6.7. CPU

Use structure modeling to connect input and output of modules following the data path in Figure 1.

1.7. Reminder

Lab 2 and 3 will be strongly related to this Lab. Please make sure you can fully understand how to write this homework; otherwise you may encounter difficulties in your future labs. Also, because this homework is rather simple, it is recommended for you to get familiar to waveform visualization tool (e.g. gtkwave), which is much more useful than “display method” (or printf大法 in C, cout大法 in C++, which only prints messages on terminal rather than using debugger to trace, stepwise execution, etc.). You may not have enough time to learn this tool at the labs, or hard to learn it from scratch because of the difficulty of the labs.

2. Report

2.1. Modules Explanation

You should briefly explain how the modules you implement work in the report. You have to explain them in human-readable sentences. Either English or Chinese is welcome, but no Verilog. Explaining Verilog modules in Verilog is nonsense. Simply pasting your codes into report with no or little explanation will get zero points for the report. You have to write more detail than Section 1.6.

Take “PC.v” as example, an acceptable report would be:

PC module reads clock signals, reset bit, start bit, and next cycle PC as input, and outputs the PC of current cycle. This module changes its internal register “pc_o” at positive edge of clock signal. When reset signal is set, PC is reset to 0. And PC will only be updated by next PC when start bit is on.

And following report will get zero points.

The inputs of PC are clk_i, rst_i, pc_i, and output pc_o.
It works as follows:

```
always@(posedge clk_i or negedge rst_i) begin
    if(~rst_i) begin
        pc_o <= 32'b0;
    end
    else begin
        pc_o <= pc_i;
    end
end
end
```

2.2. Development Environment

Please specify the OS (e.g. MacOS, Windows, Ubuntu 20.04) and compiler (e.g. iverilog) or IDE (e.g. ModelSim) you use in the report, in case that we cannot reproduce the same result as the one in your computer.

3. Environment

Requirement: Docker

After you unzip the supplied file, we will get a directory in the following structure

- Lab1/
 - Lab1_spec.pdf
 - Lab1_slide.pdf
 - Lab1/
 - ◆ Makefile
 - ◆ code/
 - src/
 - <Implement your CPU here>
 - supplied/
 - <supplied codes, don't modify them>
 - ◆ Docker-compose.yml

- ◆ Dockerfile
- ◆ Judge.yaml
- ◆ Testcases/
 - <sample testcases>
- ◆ Log/
 - <logs>

You should modify the codes in “code/src” only and do not modify anything in “code/supplied”. The sample testcases are listed in the directory “testcases”.

After implemented your CPU, use `$make` or `$docker-compose up` to execute your code and get the log and report. Docker-compose will build up the environment for you. You can find the log, text and waveform, in the directory “log” after each execution.

If you don't have docker in your environment. The alternative is using the following commands

```
$cp testcases/instruction_n.txt instruction.txt
$iverilog -o cpu code/src/*.v code/supplied/*.v
$vpv cpu
```

And compare the file “output.txt” with the corresponding output_n.txt

We recommend develop under the provided environment, otherwise, please make sure your code run correctly under **ubuntu 22.04** with **iverilog=11.0-1.1**. **You will get 0 point if your code cannot be executed correctly on our environment.**

4. Submission Rules

Copy all your Verilog codes in “code/src” into a directory named “src”, then put “src” and your report (should be named in format “studentID_lab1_report.pdf”, e.g. “b09902000_lab1_report.pdf”) into a directory named “studentID_lab1”. **Please note that you don't have to include any other files provided by the TA, such as testbench.v, Instruction_Memory.v, Registers.v, PC.v, instruction.txt, and output.txt, in your submission.** Finally, zip this directory, and upload this zip file onto NTU COOL before **11/05/2024 (Tue.) 23:59**.

In short, we should see a single directory like following structure after we type

```
$ unzip b11902000_lab1.zip
```

in Linux terminal:

- b11902000_lab1/
 - o b11902000_lab1/src
 - b11902000_lab1/src/CPU.v
 - b11902000_lab1/src/ALU.v
 - ...
 - o b11902000_lab1/ b11902000_lab1_report.pdf

Make sure you didn't includes the following files in your submission:
Instruction Memory.v, PC.v, Registers.v, testbench.v, instruction.txt, output.txt.

5. Evaluation Criteria

5.1. Programming Part (80%)

5.2. Report (20%)

5.3. Other

Minor mistakes (examples below) causing compilation error: -10 pts

- o wrong usage of “include”
- o submitting unnecessary files (those provided by TA except CPU.v)
- o other mistakes that can be fixed within 5 lines

Major mistakes causing compilation error: 0 pts on programming part

Wrong directory format: -10 pts

Late submission: -10 pts per day

email to ntu.eclab.ca.ta@gmail.com if you have any questions.